
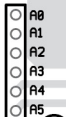


ARDUINO UNO




D1-D8 = 1N4007
J1-J7 = JUMPER WIRES

9723H

CON4

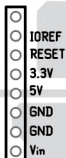

CON1
FOR
MPU-6050

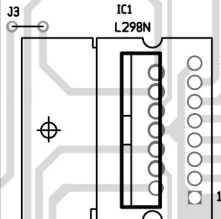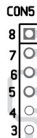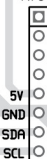

J4

J5

J6



J7



S1
ON/OFF



BATT.1
12V

